

REVIEW QUESTIONS

- 10.1** The voltage V_o across the capacitor in Fig. 10.43 is:
 (a) $5 \angle 0^\circ$ V (b) $7.071 \angle 45^\circ$ V
 (c) $7.071 \angle -45^\circ$ V (d) $5 \angle -45^\circ$ V

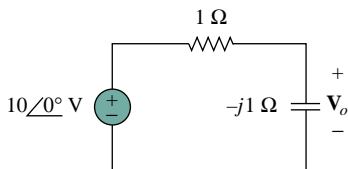


Figure 10.43 For Review Question 10.1.

- 10.2** The value of the current I_o in the circuit in Fig. 10.44 is:
 (a) $4 \angle 0^\circ$ A (b) $2.4 \angle -90^\circ$ A
 (c) $0.6 \angle 0^\circ$ A (d) -1 A

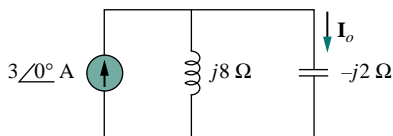


Figure 10.44 For Review Question 10.2.

- 10.3** Using nodal analysis, the value of V_o in the circuit of Fig. 10.45 is:
 (a) -24 V (b) -8 V
 (c) 8 V (d) 24 V

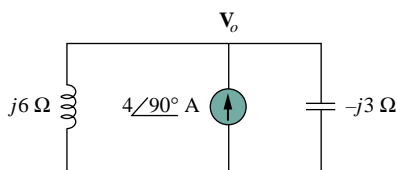


Figure 10.45 For Review Question 10.3.

- 10.4** In the circuit of Fig. 10.46, current $i(t)$ is:
 (a) $10 \cos t$ A (b) $10 \sin t$ A (c) $5 \cos t$ A
 (d) $5 \sin t$ A (e) $4.472 \cos(t - 63.43^\circ)$ A

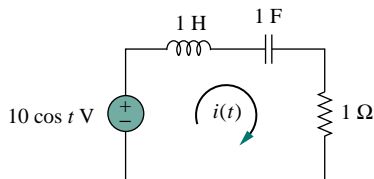


Figure 10.46 For Review Question 10.4.

- 10.5** Refer to the circuit in Fig. 10.47 and observe that the two sources do not have the same frequency. The current $i_x(t)$ can be obtained by:
 (a) source transformation
 (b) the superposition theorem
 (c) PSpice

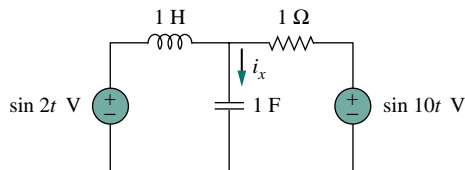


Figure 10.47 For Review Question 10.5.

- 10.6** For the circuit in Fig. 10.48, the Thevenin impedance at terminals $a-b$ is:
 (a) 1Ω (b) $0.5 - j0.5 \Omega$
 (c) $0.5 + j0.5 \Omega$ (d) $1 + j2 \Omega$
 (e) $1 - j2 \Omega$

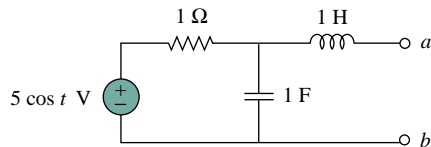


Figure 10.48 For Review Questions 10.6 and 10.7.

- 10.7** In the circuit of Fig. 10.48, the Thevenin voltage at terminals $a-b$ is:
 (a) $3.535 \angle -45^\circ$ V (b) $3.535 \angle 45^\circ$ V
 (c) $7.071 \angle -45^\circ$ V (d) $7.071 \angle 45^\circ$ V

- 10.8** Refer to the circuit in Fig. 10.49. The Norton equivalent impedance at terminals $a-b$ is:
 (a) $-j4 \Omega$ (b) $-j2 \Omega$
 (c) $j2 \Omega$ (d) $j4 \Omega$

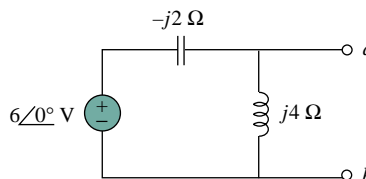


Figure 10.49 For Review Questions 10.8 and 10.9.

10.9 The Norton current at terminals a - b in the circuit of Fig. 10.49 is:

- (a) $1 \angle 0^\circ$ A (b) $1.5 \angle -90^\circ$ A
 (c) $1.5 \angle 90^\circ$ A (d) $3 \angle 90^\circ$ A

10.10 *PSpice* can handle a circuit with two independent sources of different frequencies.

- (a) True (b) False

Answers: 10.1c, 10.2a, 10.3d, 10.4a, 10.5b, 10.6c, 10.7a, 10.8a, 10.9d, 10.10b.

PROBLEMS

Section 10.2 Nodal Analysis

10.1 Find v_o in the circuit in Fig. 10.50.

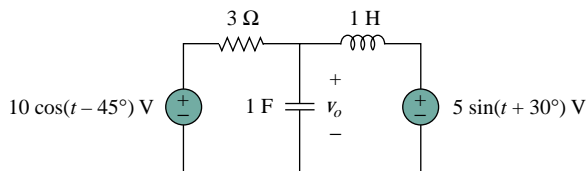


Figure 10.50 For Prob. 10.1.

10.2 For the circuit depicted in Fig. 10.51 below, determine i_o .

10.3 Determine v_o in the circuit of Fig. 10.52.

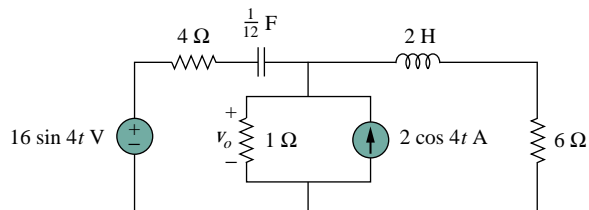


Figure 10.52 For Prob. 10.3.

10.4 Compute $v_o(t)$ in the circuit of Fig. 10.53.

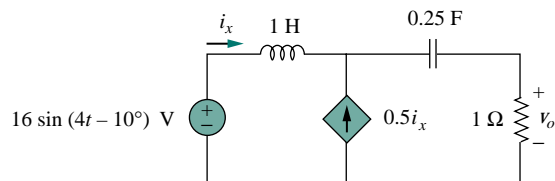


Figure 10.53 For Prob. 10.4.

10.5 Use nodal analysis to find v_o in the circuit of Fig. 10.54.

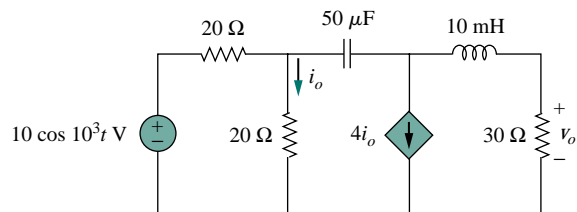


Figure 10.54 For Prob. 10.5.

10.6 Using nodal analysis, find $i_o(t)$ in the circuit in Fig. 10.55.

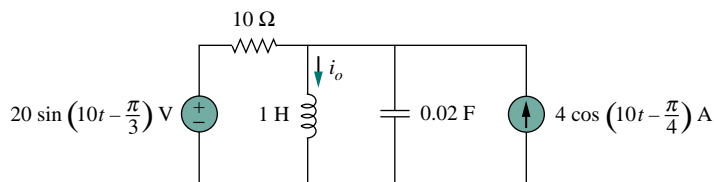


Figure 10.51 For Prob. 10.2.

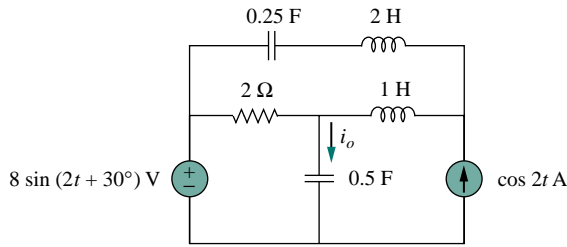


Figure 10.55 For Prob. 10.6.

10.7 By nodal analysis, find i_o in the circuit in Fig. 10.56.

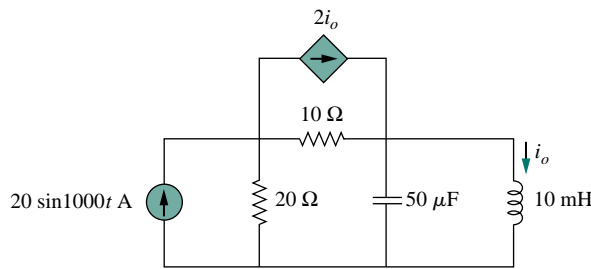


Figure 10.56 For Prob. 10.7.

10.8 Calculate the voltage at nodes 1 and 2 in the circuit of Fig. 10.57 using nodal analysis.

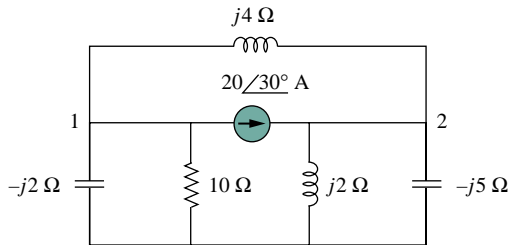


Figure 10.57 For Prob. 10.8.

10.9 Solve for the current I in the circuit of Fig. 10.58 using nodal analysis.

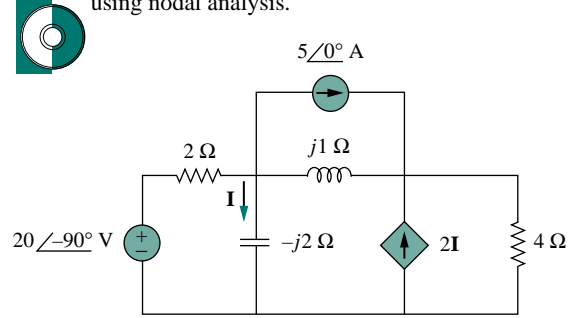


Figure 10.58 For Prob. 10.9.

10.10 Using nodal analysis, find V_1 and V_2 in the circuit of Fig. 10.59.

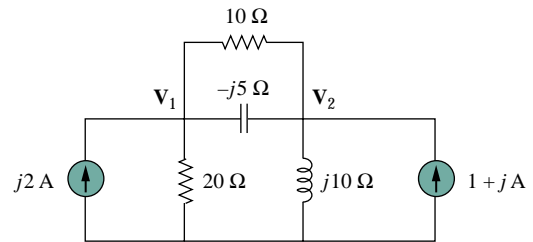


Figure 10.59 For Prob. 10.10.

10.11 By nodal analysis, obtain current I_o in the circuit in Fig. 10.60.

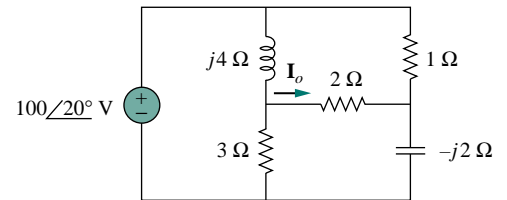


Figure 10.60 For Prob. 10.11.

10.12 Use nodal analysis to obtain V_o in the circuit of Fig. 10.61 below.

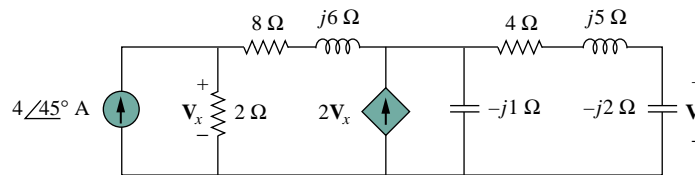


Figure 10.61 For Prob. 10.12.

10.13 Obtain V_o in Fig. 10.62 using nodal analysis.

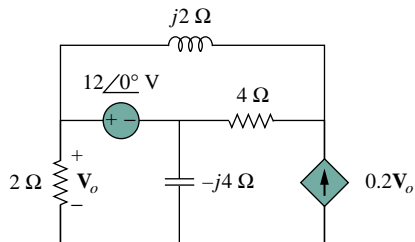


Figure 10.62 For Prob. 10.13.

10.14 Refer to Fig. 10.63. If $v_s(t) = V_m \sin \omega t$ and $v_o(t) = A \sin(\omega t + \phi)$, derive the expressions for A and ϕ .

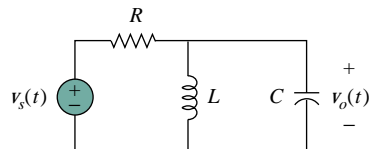


Figure 10.63 For Prob. 10.14.

10.15 For each of the circuits in Fig. 10.64, find V_o/V_i for $\omega = 0$, $\omega \rightarrow \infty$, and $\omega^2 = 1/LC$.

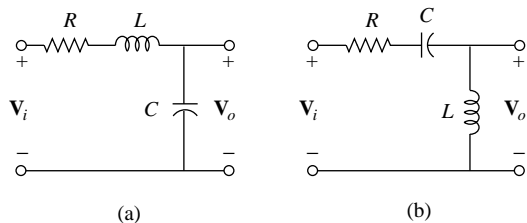


Figure 10.64 For Prob. 10.15.

10.16 For the circuit in Fig. 10.65, determine V_o/V_s .

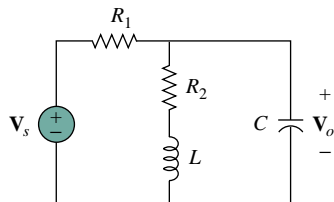


Figure 10.65 For Prob. 10.16.

Section 10.3 Mesh Analysis

10.17 Obtain the mesh currents I_1 and I_2 in the circuit of Fig. 10.66.

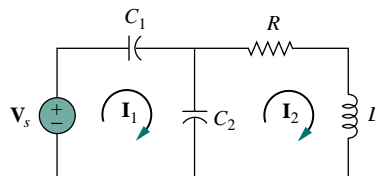


Figure 10.66 For Prob. 10.17.

10.18 Solve for i_o in Fig. 10.67 using mesh analysis.

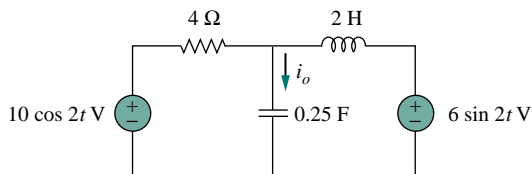


Figure 10.67 For Prob. 10.18.

10.19 Rework Prob. 10.5 using mesh analysis.

10.20 Using mesh analysis, find I_1 and I_2 in the circuit of Fig. 10.68.

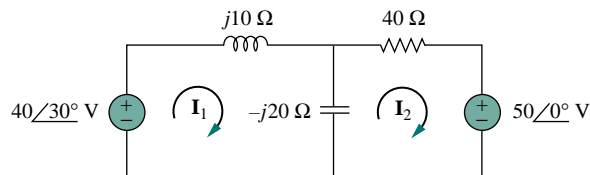


Figure 10.68 For Prob. 10.20.

10.21 By using mesh analysis, find I_1 and I_2 in the circuit depicted in Fig. 10.69.

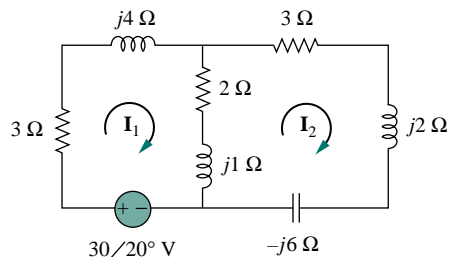


Figure 10.69 For Prob. 10.21.

- 10.22 Repeat Prob. 10.11 using mesh analysis.
- 10.23 Use mesh analysis to determine current I_o in the circuit of Fig. 10.70 below.
- 10.24 Determine V_o and I_o in the circuit of Fig. 10.71 using mesh analysis.

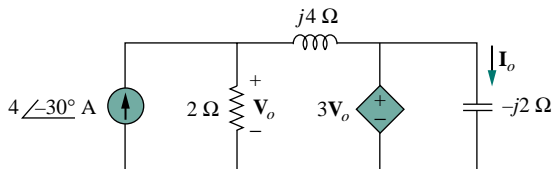


Figure 10.71 For Prob. 10.24.

- 10.25 Compute I in Prob. 10.9 using mesh analysis.
- 10.26 Use mesh analysis to find I_o in Fig. 10.28 (for Example 10.10).
- 10.27 Calculate I_o in Fig. 10.30 (for Practice Prob. 10.10) using mesh analysis.
- 10.28 Compute V_o in the circuit of Fig. 10.72 using mesh analysis.

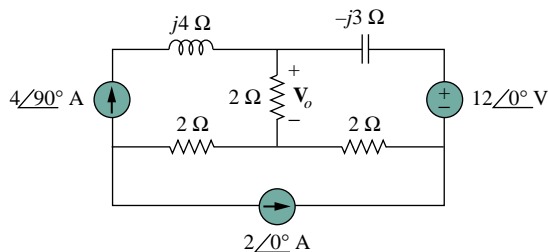


Figure 10.72 For Prob. 10.28.

- 10.29 Using mesh analysis, obtain I_o in the circuit shown in Fig. 10.73.

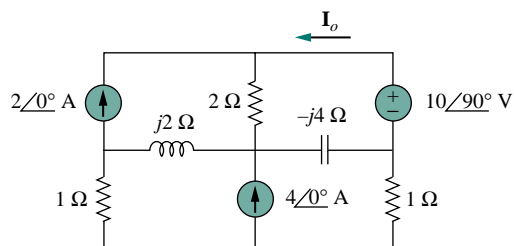


Figure 10.73 For Prob. 10.29.

Section 10.4 Superposition Theorem

- 10.30 Find i_o in the circuit shown in Fig. 10.74 using superposition.

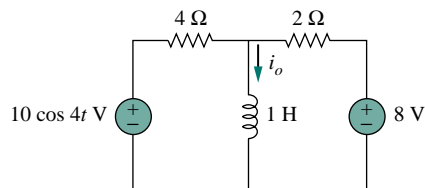


Figure 10.74 For Prob. 10.30.

- 10.31 Using the superposition principle, find i_x in the circuit of Fig. 10.75.

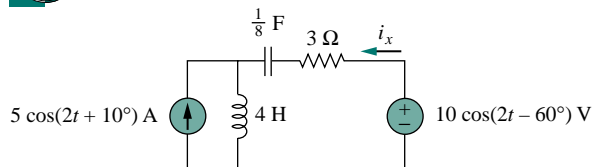


Figure 10.75 For Prob. 10.31.

- 10.32 Rework Prob. 10.2 using the superposition theorem.
- 10.33 Solve for $v_o(t)$ in the circuit of Fig. 10.76 using the superposition principle.

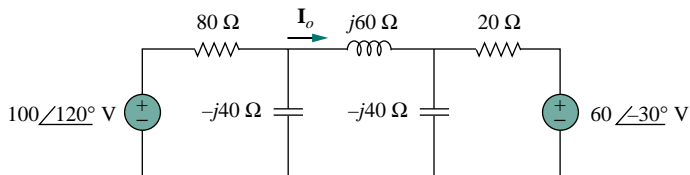


Figure 10.70 For Prob. 10.23.

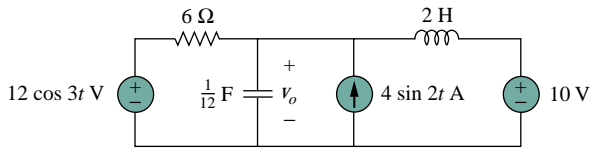


Figure 10.76 For Prob. 10.33.

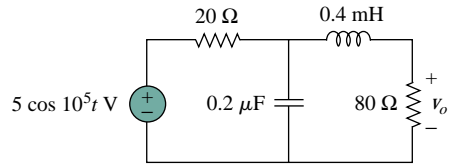


Figure 10.80 For Prob. 10.37.

10.34 Determine i_o in the circuit of Fig. 10.77.

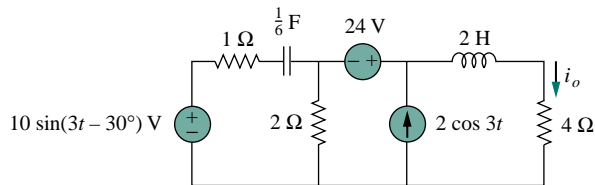


Figure 10.77 For Prob. 10.34.

10.35 Find i_o in the circuit in Fig. 10.78 using superposition.

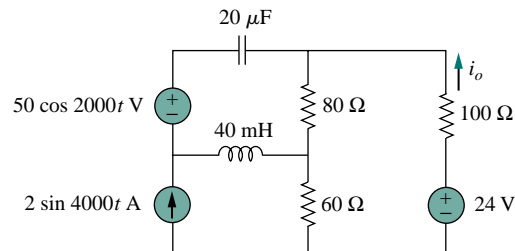


Figure 10.78 For Prob. 10.35.

Section 10.5 Source Transformation

10.36 Using source transformation, find i in the circuit of Fig. 10.79.

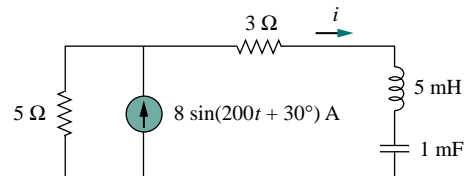


Figure 10.79 For Prob. 10.36.

10.37 Use source transformation to find v_o in the circuit in Fig. 10.80.

10.38 Solve Prob. 10.20 using source transformation.

10.39 Use the method of source transformation to find \mathbf{I}_x in the circuit of Fig. 10.81.

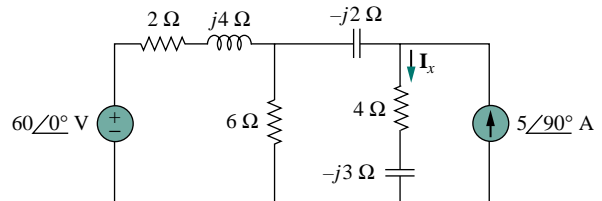


Figure 10.81 For Prob. 10.39.

10.40 Use the concept of source transformation to find \mathbf{V}_o in the circuit of Fig. 10.82.

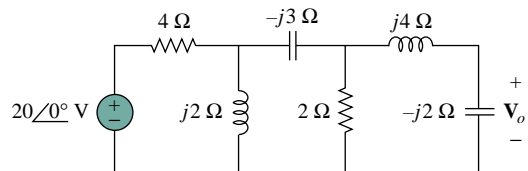


Figure 10.82 For Prob. 10.40.

Section 10.6 Thevenin and Norton Equivalent Circuits

10.41 Find the Thevenin and Norton equivalent circuits at terminals a - b for each of the circuits in Fig. 10.83.

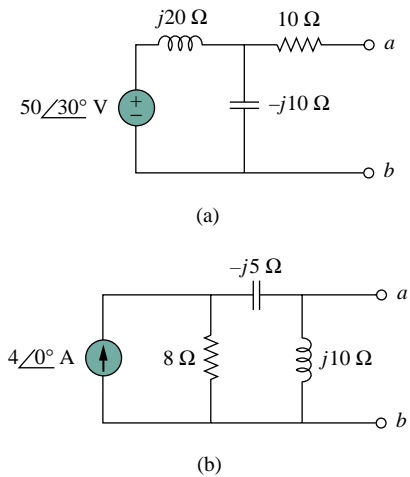


Figure 10.83 For Prob. 10.41.

- 10.42** For each of the circuits in Fig. 10.84, obtain Thevenin and Norton equivalent circuits at terminals a - b .

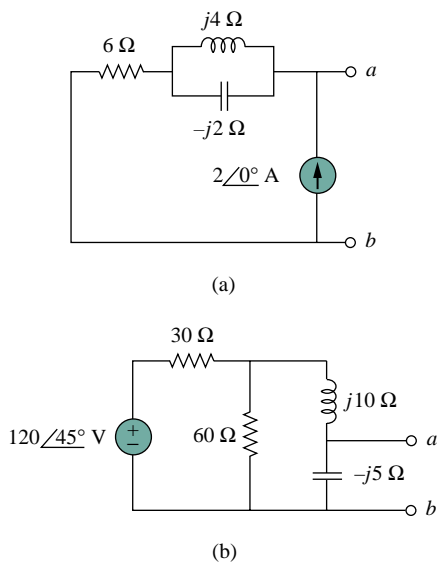


Figure 10.84 For Prob. 10.42.

- 10.43** Find the Thevenin and Norton equivalent circuits for the circuit shown in Fig. 10.85.

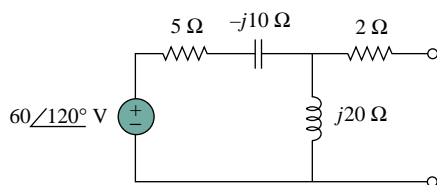


Figure 10.85 For Prob. 10.43.

- 10.44** For the circuit depicted in Fig. 10.86, find the Thevenin equivalent circuit at terminals a - b .

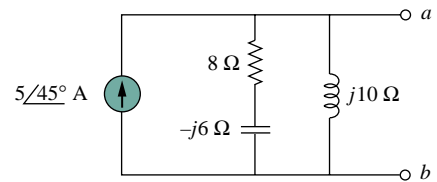


Figure 10.86 For Prob. 10.44.

- 10.45** Repeat Prob. 10.1 using Thevenin's theorem.

- 10.46** Find the Thevenin equivalent of the circuit in Fig. 10.87 as seen from:



(a) terminals a - b (b) terminals c - d

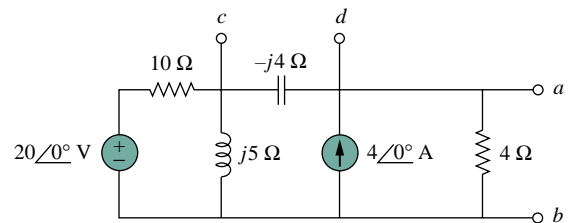


Figure 10.87 For Prob. 10.46.

- 10.47** Solve Prob. 10.3 using Thevenin's theorem.

- 10.48** Using Thevenin's theorem, find v_o in the circuit in Fig. 10.88.

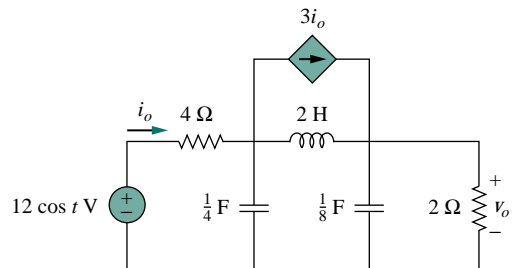


Figure 10.88 For Prob. 10.48.

- 10.49** Obtain the Norton equivalent of the circuit depicted in Fig. 10.89 at terminals a - b .

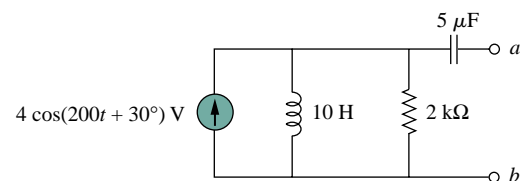


Figure 10.89 For Prob. 10.49.

- 10.50** For the circuit shown in Fig. 10.90, find the Norton equivalent circuit at terminals a - b .

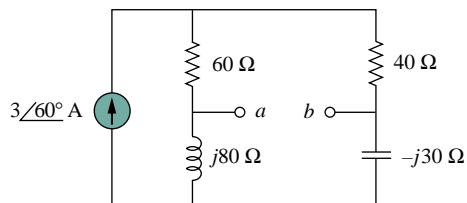


Figure 10.90 For Prob. 10.50.

- 10.51** Compute i_o in Fig. 10.91 using Norton's theorem.

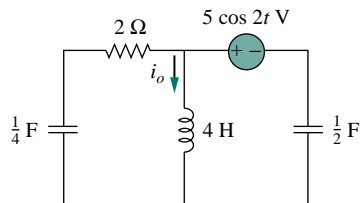


Figure 10.91 For Prob. 10.51.

- 10.52** At terminals a - b , obtain Thevenin and Norton equivalent circuits for the network depicted in Fig. 10.92. Take $\omega = 10$ rad/s.

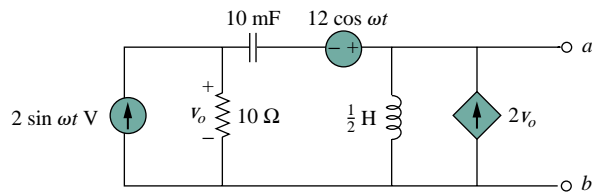


Figure 10.92 For Prob. 10.52.

Section 10.7 Op Amp AC Circuits

- 10.53** For the differentiator shown in Fig. 10.93, obtain $\mathbf{V}_o/\mathbf{V}_s$. Find $v_o(t)$ when $v_s(t) = V_m \sin \omega t$ and $\omega = 1/RC$.

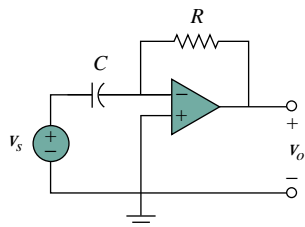


Figure 10.93 For Prob. 10.53.

- 10.54** The circuit in Fig. 10.94 is an integrator with a feedback resistor. Calculate $v_o(t)$ if $v_s = 2 \cos 4 \times 10^4 t$ V.

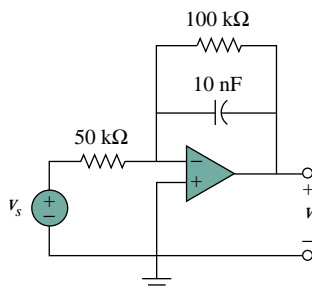


Figure 10.94 For Prob. 10.54.

- 10.55** Compute $i_o(t)$ in the op amp circuit in Fig. 10.95 if $v_s = 4 \cos 10^4 t$ V.

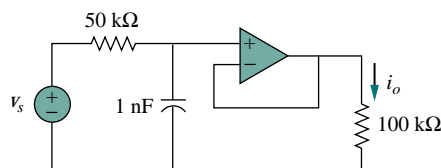


Figure 10.95 For Prob. 10.55.

- 10.56** If the input impedance is defined as $\mathbf{Z}_{in} = \mathbf{V}_s/\mathbf{I}_s$, find the input impedance of the op amp circuit in Fig. 10.96 when $R_1 = 10$ kΩ, $R_2 = 20$ kΩ, $C_1 = 10$ nF, $C_2 = 20$ nF, and $\omega = 5000$ rad/s.

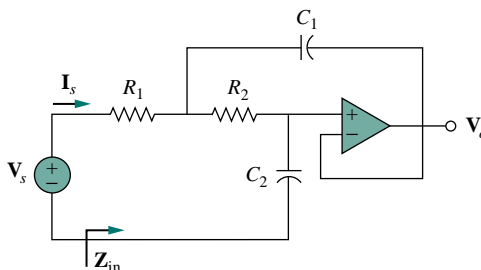


Figure 10.96 For Prob. 10.56.

- 10.57** Evaluate the voltage gain $\mathbf{A}_v = \mathbf{V}_o/\mathbf{V}_s$ in the op amp circuit of Fig. 10.97. Find \mathbf{A}_v at $\omega = 0$, $\omega \rightarrow \infty$, $\omega = 1/R_1 C_1$, and $\omega = 1/R_2 C_2$.

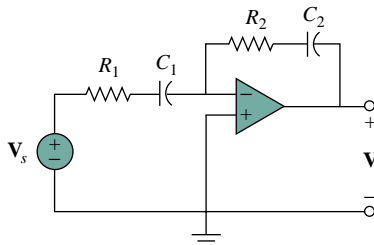


Figure 10.97 For Prob. 10.57.

- 10.58** In the op amp circuit of Fig. 10.98, find the closed-loop gain and phase shift if $C_1 = C_2 = 1$ nF, $R_1 = R_2 = 100$ k Ω , $R_3 = 20$ k Ω , $R_4 = 40$ k Ω , and $\omega = 2000$ rad/s.

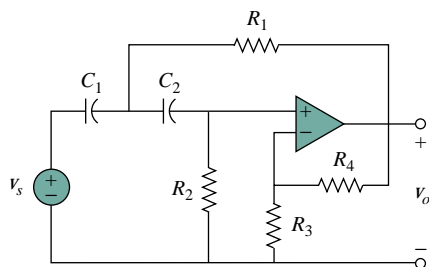


Figure 10.98 For Prob. 10.58.

- 10.59** Compute the closed-loop gain V_o/V_s for the op amp circuit of Fig. 10.99.

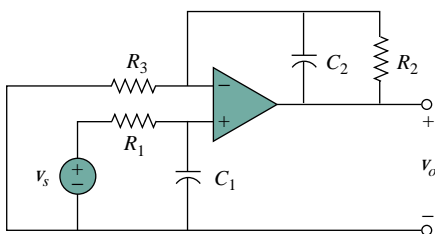


Figure 10.99 For Prob. 10.59.

- 10.60** Determine $v_o(t)$ in the op amp circuit in Fig. 10.100 below.

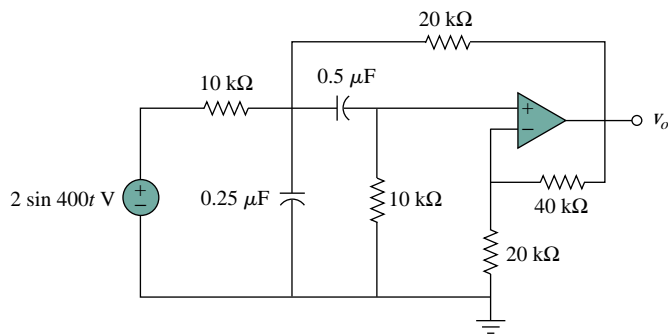


Figure 10.100 For Prob. 10.60.

- 10.61** For the op amp circuit in Fig. 10.101, obtain $v_o(t)$.

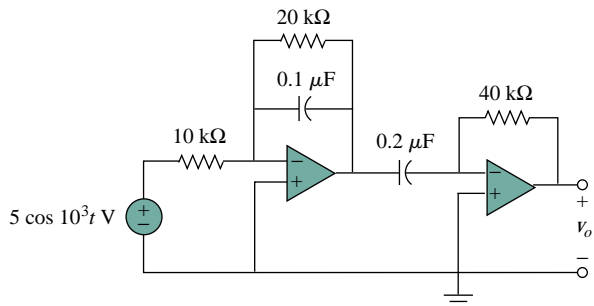


Figure 10.101 For Prob. 10.61.

- 10.62** Obtain $v_o(t)$ for the op amp circuit in Fig. 10.102 if $v_s = 4 \cos(1000t - 60^\circ)$ V.

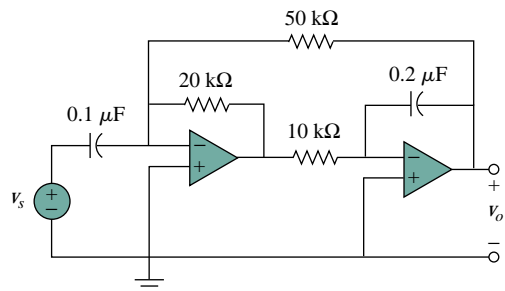


Figure 10.102 For Prob. 10.62.

Section 10.8 AC Analysis Using PSpice

- 10.63** Use PSpice to solve Example 10.10.
10.64 Solve Prob. 10.13 using PSpice.

10.65 Obtain V_o in the circuit of Fig. 10.103 using *PSpice*.

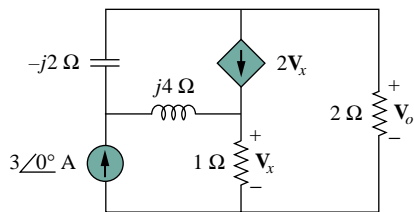


Figure 10.103 For Prob. 10.65.

10.66 Use *PSpice* to find V_1 , V_2 , and V_3 in the network of Fig. 10.104.

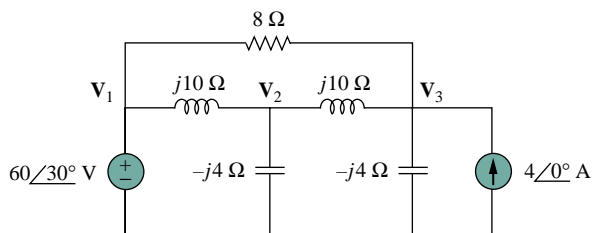


Figure 10.104 For Prob. 10.66.

10.67 Determine V_1 , V_2 , and V_3 in the circuit of Fig. 10.105 using *PSpice*.

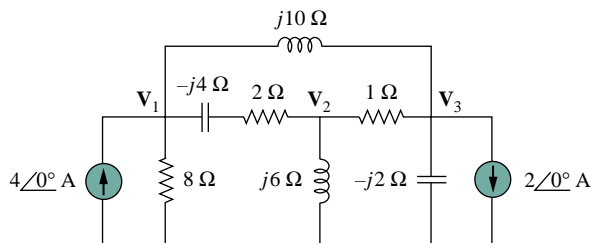


Figure 10.105 For Prob. 10.67.

10.68 Use *PSpice* to find v_o and i_o in the circuit of Fig. 10.106 below.

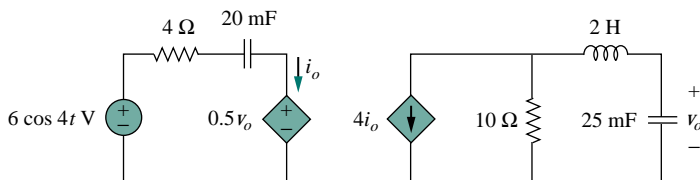


Figure 10.106 For Prob. 10.68.

Section 10.9 Applications

10.69 The op amp circuit in Fig. 10.107 is called an *inductance simulator*. Show that the input impedance is given by

$$Z_{in} = \frac{V_{in}}{I_{in}} = j\omega L_{eq}$$

where

$$L_{eq} = \frac{R_1 R_3 R_4}{R_2} C$$

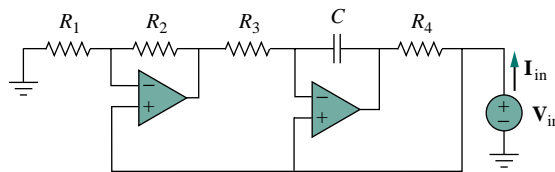


Figure 10.107 For Prob. 10.69.

10.70 Figure 10.108 shows a Wien-bridge network. Show that the frequency at which the phase shift between the input and output signals is zero is $f = \frac{1}{2}\pi RC$, and that the necessary gain is $A_v = V_o/V_i = 3$ at that frequency.

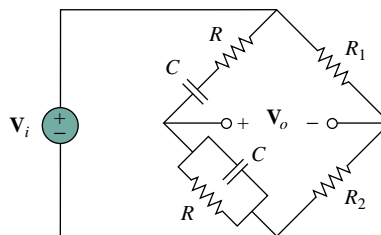


Figure 10.108 For Prob. 10.70.

10.71 Consider the oscillator in Fig. 10.109.
(a) Determine the oscillation frequency.

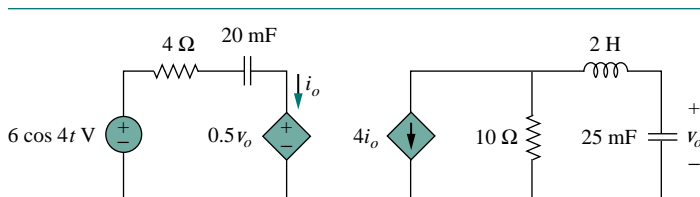


Figure 10.106 For Prob. 10.68.



(b) Obtain the minimum value of R for which oscillation takes place.

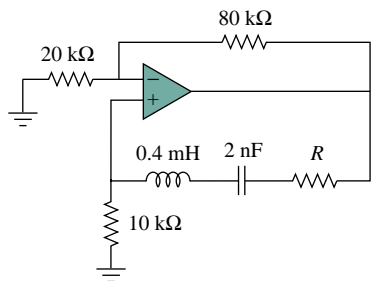


Figure 10.109 For Prob. 10.71.

10.72 The oscillator circuit in Fig. 10.110 uses an ideal op amp.



- (a) Calculate the minimum value of R_o that will cause oscillation to occur.
- (b) Find the frequency of oscillation.

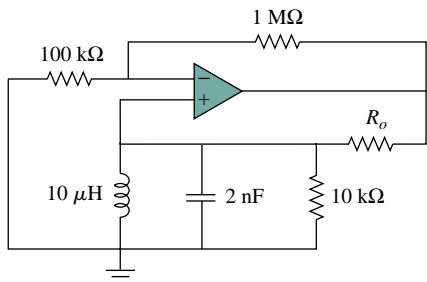


Figure 10.110 For Prob. 10.72.

10.73 Figure 10.111 shows a *Colpitts oscillator*. Show that the oscillation frequency is

$$f_o = \frac{1}{2\pi\sqrt{LC_T}}$$

where $C_T = C_1C_2/(C_1 + C_2)$. Assume $R_i \gg X_{C_2}$.

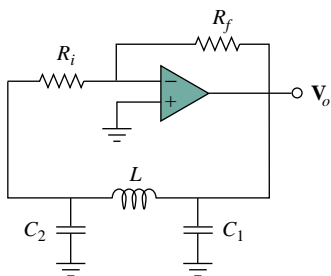


Figure 10.111 A Colpitts oscillator; for Prob. 10.73.

(Hint: Set the imaginary part of the impedance in the feedback circuit equal to zero.)

10.74 Design a Colpitts oscillator that will operate at 50 kHz.

10.75 Figure 10.112 shows a *Hartley oscillator*. Show that the frequency of oscillation is

$$f_o = \frac{1}{2\pi\sqrt{C(L_1 + L_2)}}$$

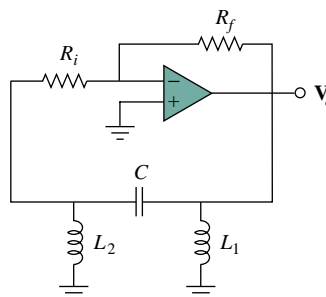


Figure 10.112 A Hartley oscillator; for Prob. 10.75.

10.76 Refer to the oscillator in Fig. 10.113.

(a) Show that

$$\frac{V_2}{V_o} = \frac{1}{3 + j(\omega L/R - R/\omega L)}$$

(b) Determine the oscillation frequency f_o .

(c) Obtain the relationship between R_1 and R_2 in order for oscillation to occur.

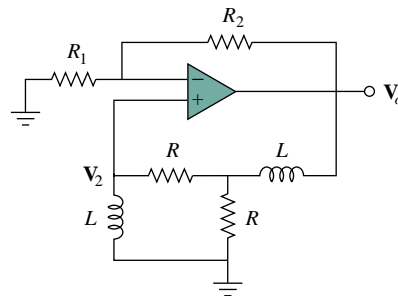


Figure 10.113 For Prob. 10.76.