

- 13.9** In order to match a source with internal impedance of  $500\ \Omega$  to a  $15\text{-}\Omega$  load, what is needed is:
- (a) step-up linear transformer
  - (b) step-down linear transformer
  - (c) step-up ideal transformer
  - (d) step-down ideal transformer
  - (e) autotransformer

- 13.10** Which of these transformers can be used as an isolation device?
- (a) linear transformer
  - (b) ideal transformer
  - (c) autotransformer
  - (d) all of the above

Answers: 13.1b, 13.2a, 13.3b, 13.4b, 13.5d, 13.6b, 13.7c, 13.8a, 13.9d, 13.10b.

PROBLEMS

Section 13.2 Mutual Inductance

- 13.1** For the three coupled coils in Fig. 13.72, calculate the total inductance.

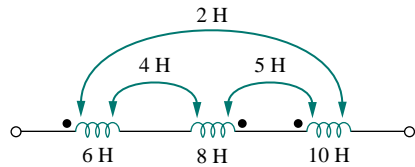


Figure 13.72 For Prob. 13.1.

- 13.2** Determine the inductance of the three series-connected inductors of Fig. 13.73.

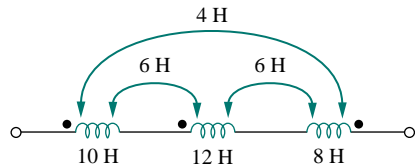


Figure 13.73 For Prob. 13.2.

- 13.3** Two coils connected in series-aiding fashion have a total inductance of 250 mH. When connected in a series-opposing configuration, the coils have a total inductance of 150 mH. If the inductance of one coil ( $L_1$ ) is three times the other, find  $L_1$ ,  $L_2$ , and  $M$ . What is the coupling coefficient?

- 13.4** (a) For the coupled coils in Fig. 13.74(a), show that  

$$L_{eq} = L_1 + L_2 + 2M$$
 (b) For the coupled coils in Fig. 13.74(b), show that

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 L_2 - 2M^2}$$

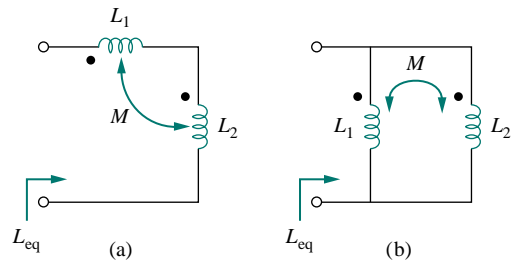


Figure 13.74 For Prob. 13.4.

- 13.5** Determine  $V_1$  and  $V_2$  in terms of  $I_1$  and  $I_2$  in the circuit in Fig. 13.75.

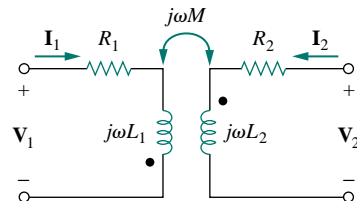


Figure 13.75 For Prob. 13.5.

- 13.6** Find  $V_o$  in the circuit of Fig. 13.76.

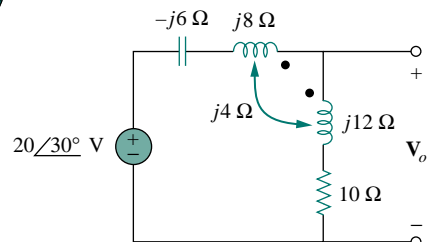


Figure 13.76 For Prob. 13.6.

- 13.7 Obtain  $V_o$  in the circuit of Fig. 13.77.

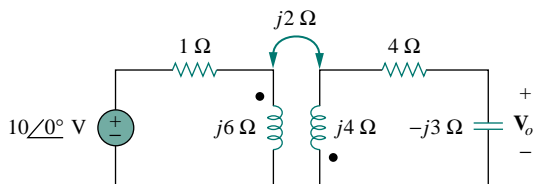


Figure 13.77 For Prob. 13.7.

- 13.8 Find  $V_x$  in the network shown in Fig. 13.78.

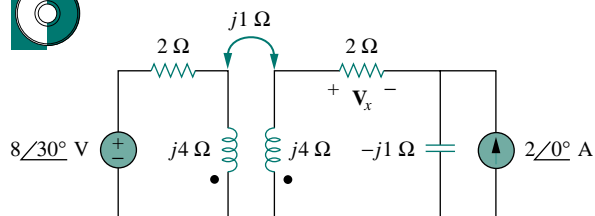


Figure 13.78 For Prob. 13.8.

- 13.9 Find  $I_o$  in the circuit of Fig. 13.79.

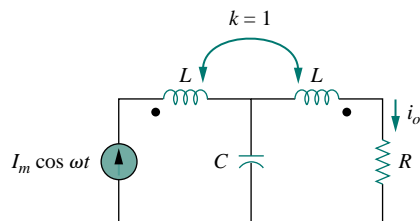


Figure 13.79 For Prob. 13.9.

- 13.10 Obtain the mesh equations for the circuit in Fig. 13.80.

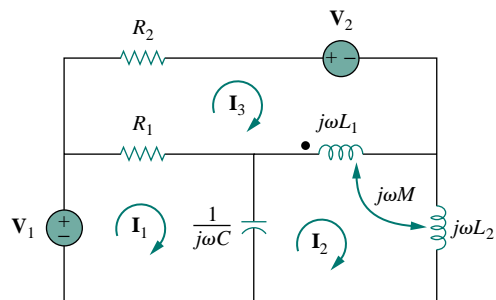


Figure 13.80 For Prob. 13.10.

- 13.11 Obtain the Thevenin equivalent circuit for the circuit in Fig. 13.81 at terminals  $a$ - $b$ .

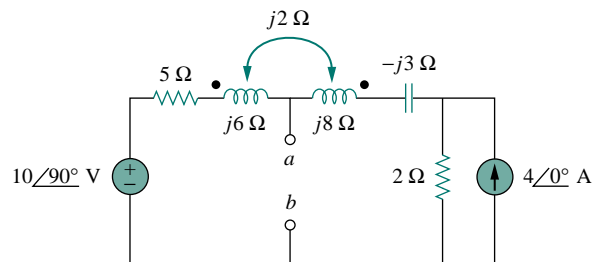


Figure 13.81 For Prob. 13.11.

- 13.12 Find the Norton equivalent for the circuit in Fig. 13.82 at terminals  $a$ - $b$ .

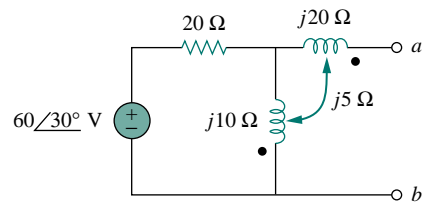


Figure 13.82 For Prob. 13.12.

### Section 13.3 Energy in a Coupled Circuit

- 13.13 Determine currents  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit of Fig. 13.83. Find the energy stored in the coupled coils at  $t = 2$  ms. Take  $\omega = 1000$  rad/s.

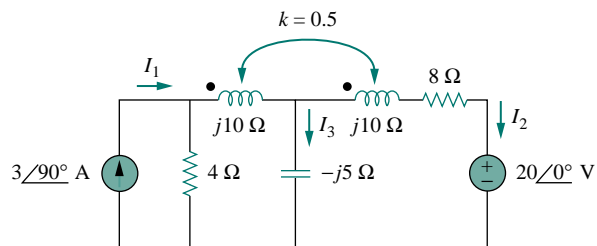


Figure 13.83 For Prob. 13.13.

- 13.14** Find  $\mathbf{I}_1$  and  $\mathbf{I}_2$  in the circuit of Fig. 13.84. Calculate the power absorbed by the  $4\text{-}\Omega$  resistor.

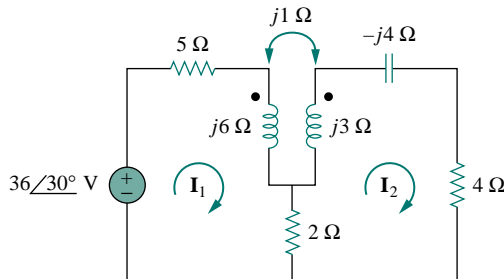


Figure 13.84 For Prob. 13.14.

- \*13.15** Find current  $\mathbf{I}_o$  in the circuit of Fig. 13.85.

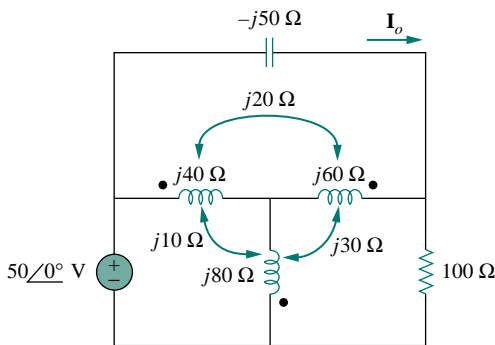


Figure 13.85 For Prob. 13.15.

- 13.16** If  $M = 0.2\text{ H}$  and  $v_s = 12 \cos 10t\text{ V}$  in the circuit of Fig. 13.86, find  $i_1$  and  $i_2$ . Calculate the energy stored in the coupled coils at  $t = 15\text{ ms}$ .

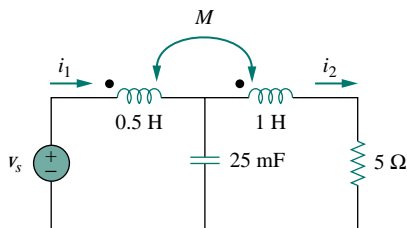


Figure 13.86 For Prob. 13.16.

- 13.17** In the circuit of Fig. 13.87, (a) find the coupling coefficient,

- (b) calculate  $v_o$ ,  
(c) determine the energy stored in the coupled inductors at  $t = 2\text{ s}$ .

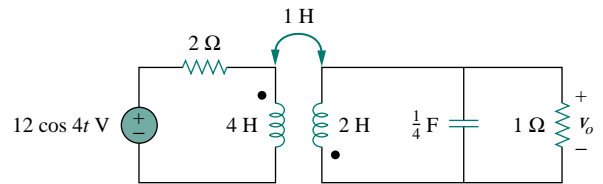


Figure 13.87 For Prob. 13.17.

- 13.18** For the network in Fig. 13.88, find  $\mathbf{Z}_{ab}$  and  $\mathbf{I}_o$ .

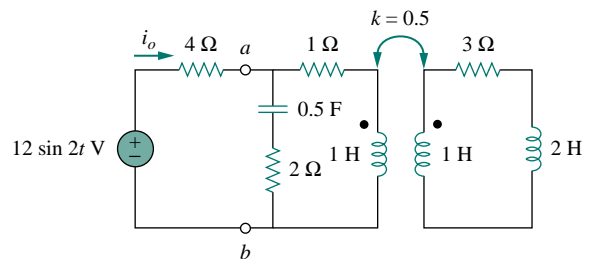


Figure 13.88 For Prob. 13.18.

- 13.19** Find  $\mathbf{I}_o$  in the circuit of Fig. 13.89. Switch the dot on the winding on the right and calculate  $\mathbf{I}_o$  again.

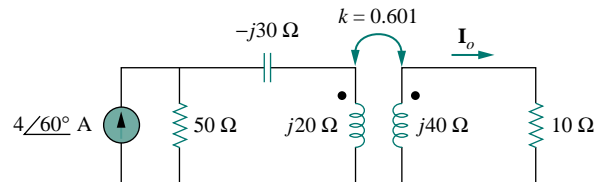


Figure 13.89 For Prob. 13.19.

- 13.20** Rework Example 13.1 using the concept of reflected impedance.

### Section 13.4 Linear Transformers

- 13.21** In the circuit of Fig. 13.90, find the value of the coupling coefficient  $k$  that will make the  $10\text{-}\Omega$  resistor dissipate  $320\text{ W}$ . For this value of  $k$ , find the energy stored in the coupled coils at  $t = 1.5\text{ s}$ .

\*An asterisk indicates a challenging problem.

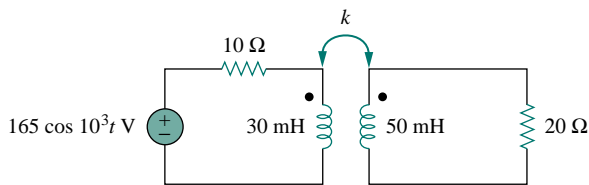


Figure 13.90 For Prob. 13.21.

- 13.22 (a) Find the input impedance of the circuit in Fig. 13.91 using the concept of reflected impedance.  
 (b) Obtain the input impedance by replacing the linear transformer by its T equivalent.

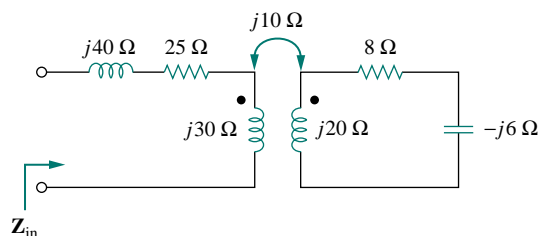


Figure 13.91 For Prob. 13.22.

- 13.23 For the circuit in Fig. 13.92, find:  
 (a) the T-equivalent circuit,  
 (b) the  $\Pi$ -equivalent circuit.

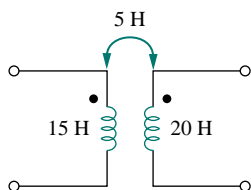


Figure 13.92 For Prob. 13.23.

- \*13.24 Two linear transformers are cascaded as shown in Fig. 13.93. Show that

$$\mathbf{Z}_{\text{in}} = \frac{\omega^2 R(L_a^2 + L_a L_b - M_a^2) + j\omega^3(L_a^2 L_b + L_a L_b^2 - L_a M_b^2 - L_b M_a^2)}{\omega^2(L_a L_b + L_b^2 - M_b^2) - j\omega R(L_a + L_b)}$$

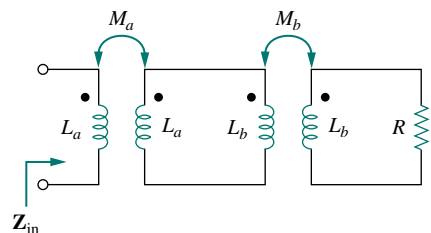


Figure 13.93 For Prob. 13.24.

- 13.25 Determine the input impedance of the air-core transformer circuit of Fig. 13.94.

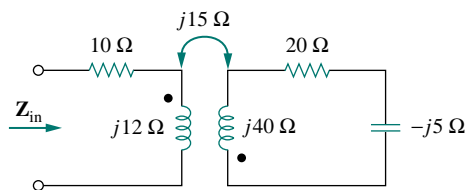


Figure 13.94 For Prob. 13.25.

### Section 13.5 Ideal Transformers

- 13.26 As done in Fig. 13.32, obtain the relationships between terminal voltages and currents for each of the ideal transformers in Fig. 13.95.

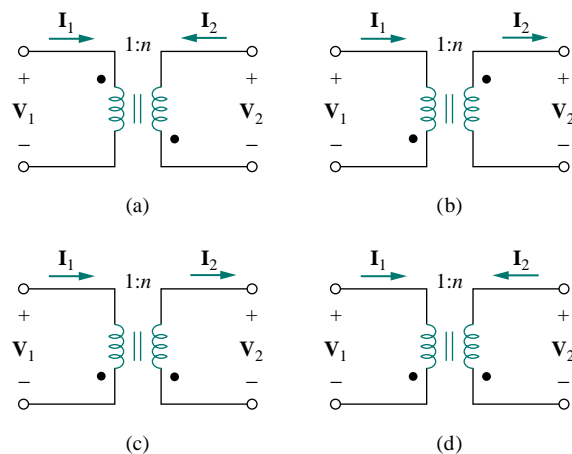


Figure 13.95 For Prob. 13.26.

- 13.27 A 4-kVA, 2300/230-V rms transformer has an equivalent impedance of  $2\angle 10^\circ \Omega$  on the primary side. If the transformer is connected to a load with 0.6 power factor leading, calculate the input impedance.

- 13.28 A 1200/240-V rms transformer has impedance  $60\angle -30^\circ \Omega$  on the high-voltage side. If the transformer is connected to a  $0.8\angle 10^\circ \Omega$  load on the low-voltage side, determine the primary and secondary currents.

- 13.29 Determine  $\mathbf{I}_1$  and  $\mathbf{I}_2$  in the circuit of Fig. 13.96.

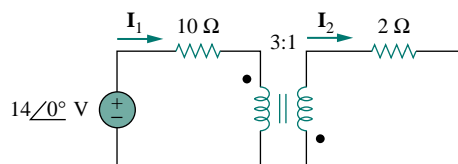


Figure 13.96 For Prob. 13.29.

**13.30** Obtain  $V_1$  and  $V_2$  in the ideal transformer circuit of Fig. 13.97.

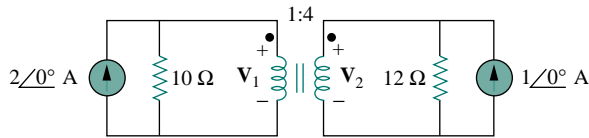


Figure 13.97 For Prob. 13.30.

**13.31** In the ideal transformer circuit of Fig. 13.98, find  $i_1(t)$  and  $i_2(t)$ .

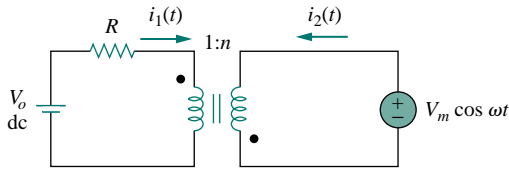


Figure 13.98 For Prob. 13.31.

**13.32** (a) Find  $I_1$  and  $I_2$  in the circuit of Fig. 13.99 below.  
(b) Switch the dot on one of the windings. Find  $I_1$  and  $I_2$  again.



**13.33** For the circuit in Fig. 13.100, find  $V_o$ . Switch the dot on the secondary side and find  $V_o$  again.

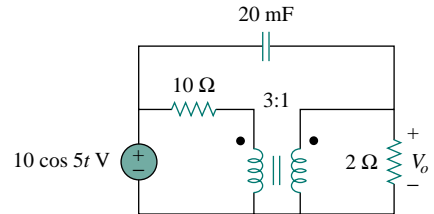


Figure 13.100 For Prob. 13.33.

**13.34** Calculate the input impedance for the network in Fig. 13.101 below.

**13.35** Use the concept of reflected impedance to find the input impedance and current  $I_1$  in Fig. 13.102 below.

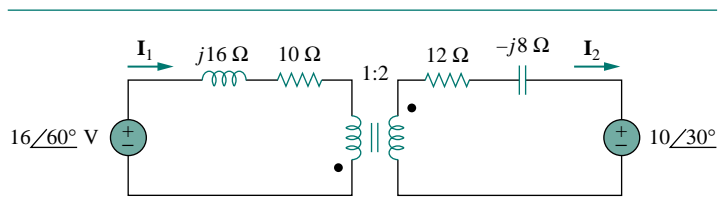


Figure 13.99 For Prob. 13.32.

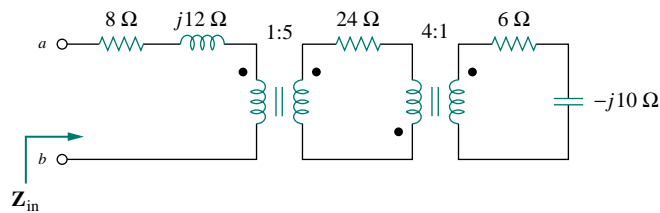


Figure 13.101 For Prob. 13.34.

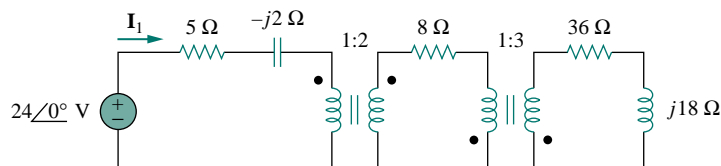


Figure 13.102 For Prob. 13.35.

- 13.36** For the circuit in Fig. 13.103, determine the turns ratio  $n$  that will cause maximum average power transfer to the load. Calculate that maximum average power.

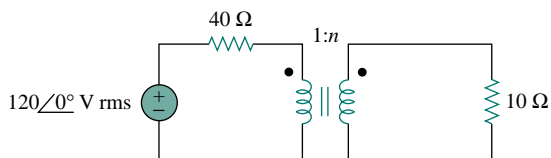


Figure 13.103 For Prob. 13.36.

- 13.37** Refer to the network in Fig. 13.104.
- Find  $n$  for maximum power supplied to the 200- $\Omega$  load.
  - Determine the power in the 200- $\Omega$  load if  $n = 10$ .

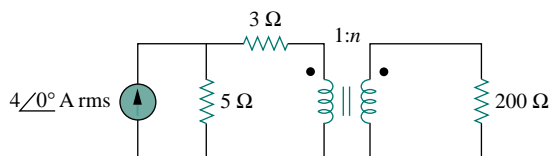


Figure 13.104 For Prob. 13.37.

- 13.38** A transformer is used to match an amplifier with an 8- $\Omega$  load as shown in Fig. 13.105. The Thevenin equivalent of the amplifier is:  $V_{Th} = 10$  V,  $Z_{Th} = 128 \Omega$ .
- Find the required turns ratio for maximum energy power transfer.

- Determine the primary and secondary currents.
- Calculate the primary and secondary voltages.

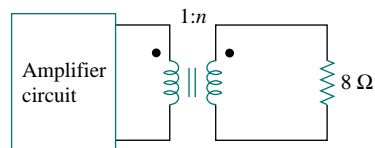


Figure 13.105 For Prob. 13.38.

- 13.39** In Fig. 13.106 below, determine the average power delivered to  $Z_s$ .

- 13.40** Find the power absorbed by the 10- $\Omega$  resistor in the ideal transformer circuit of Fig. 13.107.

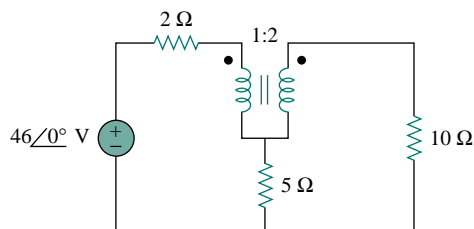


Figure 13.107 For Prob. 13.40.

- 13.41** For the ideal transformer circuit of Fig. 13.108 below, find:

- $I_1$  and  $I_2$ ,
- $V_1$ ,  $V_2$ , and  $V_o$ ,
- the complex power supplied by the source.

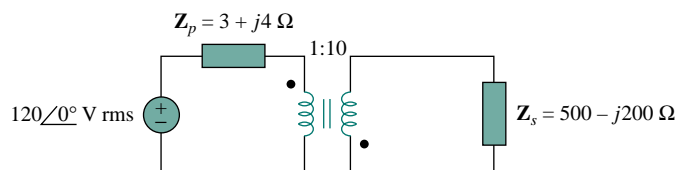


Figure 13.106 For Prob. 13.39.

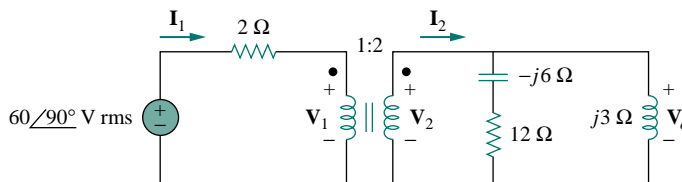


Figure 13.108 For Prob. 13.41.

- 13.42** Determine the average power absorbed by each resistor in the circuit of Fig. 13.109.

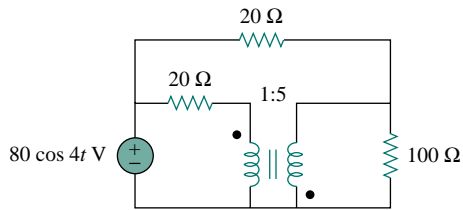


Figure 13.109 For Prob. 13.42.

- 13.43** Find the average power delivered to each resistor in the circuit of Fig. 13.110.

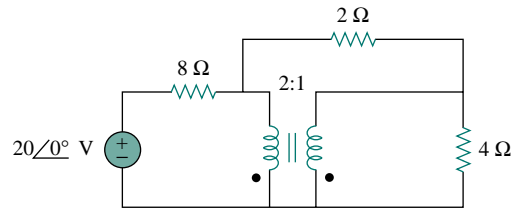


Figure 13.110 For Prob. 13.43.

- 13.44** Refer to the circuit in Fig. 13.111 below.  
 (a) Find currents  $I_1$ ,  $I_2$ , and  $I_3$ .  
 (b) Find the power dissipated in the 40-Ω resistor.
- \*13.45** For the circuit in Fig. 13.112 below, find  $I_1$ ,  $I_2$ , and  $V_o$ .
- 13.46** For the network in Fig. 13.113 below, find  
 (a) the complex power supplied by the source,  
 (b) the average power delivered to the 18-Ω resistor.

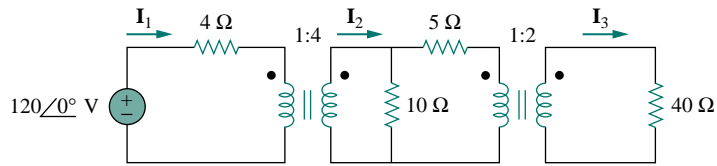


Figure 13.111 For Prob. 13.44.

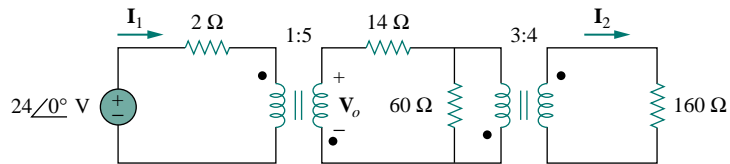


Figure 13.112 For Prob. 13.45.

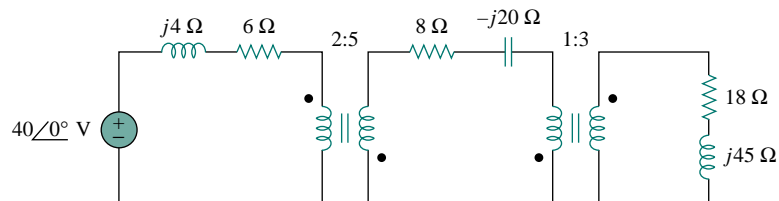


Figure 13.113 For Prob. 13.46.

- 13.47** Find the mesh currents in the circuit of Fig. 13.114 below.



### Section 13.6 Ideal Autotransformers

- 13.48** An ideal autotransformer with a 1:4 step-up turns ratio has its secondary connected to a  $120\text{-}\Omega$  load and the primary to a  $420\text{-V}$  source. Determine the primary current.
- 13.49** In the ideal autotransformer of Fig. 13.115, calculate  $\mathbf{I}_1$ ,  $\mathbf{I}_2$ , and  $\mathbf{I}_o$ . Find the average power delivered to the load.

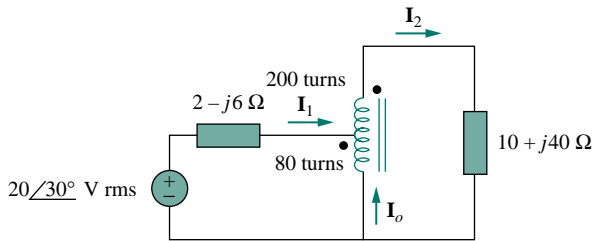


Figure 13.115 For Prob. 13.49.

- \*13.50** In the circuit of Fig. 13.116,  $\mathbf{Z}_L$  is adjusted until maximum average power is delivered to  $\mathbf{Z}_L$ . Find  $\mathbf{Z}_L$  and the maximum average power transferred to it. Take  $N_1 = 600$  turns and  $N_2 = 200$  turns.

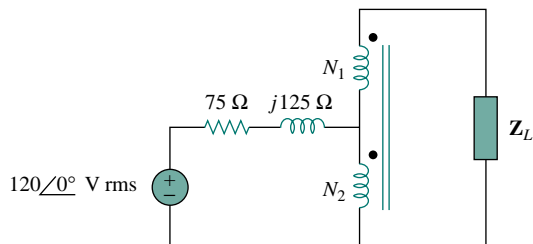


Figure 13.116 For Prob. 13.50.

- 13.51** In the ideal transformer circuit shown in Fig. 13.117, determine the average power delivered to the load.

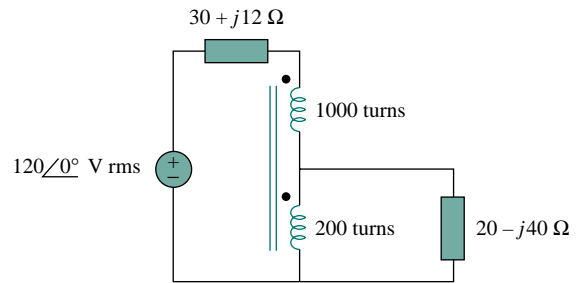


Figure 13.117 For Prob. 13.51.

- 13.52** In the autotransformer circuit in Fig. 13.118, show that

$$\mathbf{Z}_{\text{in}} = \left(1 + \frac{N_1}{N_2}\right)^2 \mathbf{Z}_L$$

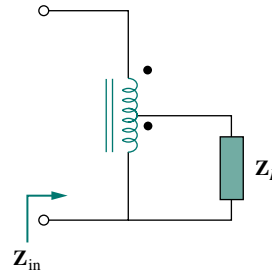


Figure 13.118 For Prob. 13.52.

### Section 13.7 Three-Phase Transformers

- 13.53** In order to meet an emergency, three single-phase transformers with  $12,470/7200$  V rms are connected in  $\Delta$ - $Y$  to form a three-phase transformer which is fed by a  $12,470\text{-V}$  transmission line. If the transformer supplies  $60$  MVA to a load, find:
- the turns ratio for each transformer,
  - the currents in the primary and secondary windings of the transformer,
  - the incoming and outgoing transmission line currents.

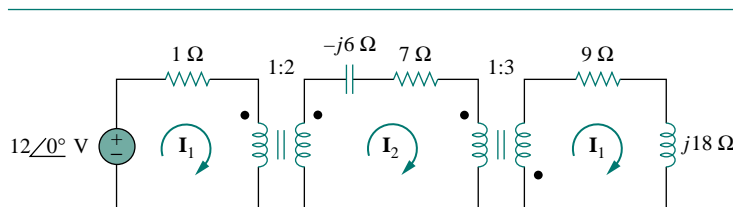


Figure 13.114 For Prob. 13.47.



- 13.54** Figure 13.119 below shows a three-phase transformer that supplies a Y-connected load.
- Identify the transformer connection.
  - Calculate currents  $I_2$  and  $I_c$ .
  - Find the average power absorbed by the load.
- 13.55** Consider the three-phase transformer shown in Fig. 13.120. The primary is fed by a three-phase source with line voltage of 2.4 kV rms, while the secondary supplies a three-phase 120-kW balanced load at pf of 0.8. Determine:
- the type of transformer connections,
  - the values of  $I_{LS}$  and  $I_{PS}$ ,
  - the values of  $I_{LP}$  and  $I_{PP}$ ,
  - the kVA rating of each phase of the transformer.
- 13.56** A balanced three-phase transformer bank with the  $\Delta$ -Y connection depicted in Fig. 13.121 below is used to step down line voltages from 4500 V rms to 900 V rms. If the transformer feeds a 120-kVA load, find:
- the turns ratio for the transformer,
  - the line currents at the primary and secondary sides.

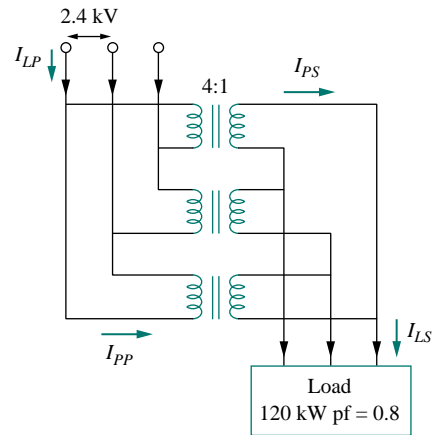


Figure 13.120 For Prob. 13.55.

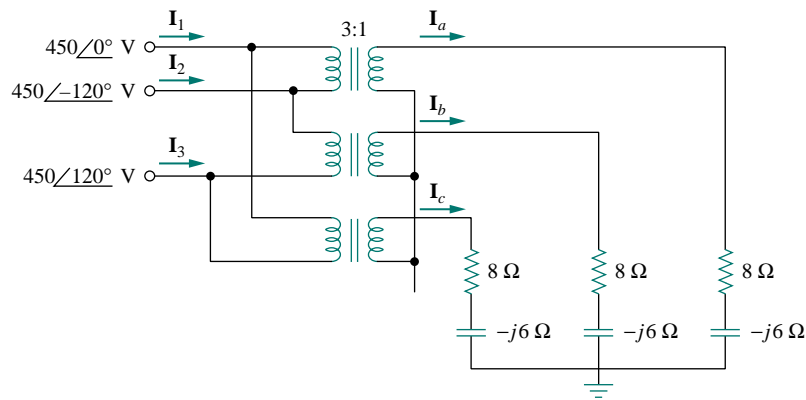


Figure 13.119 For Prob. 13.54.

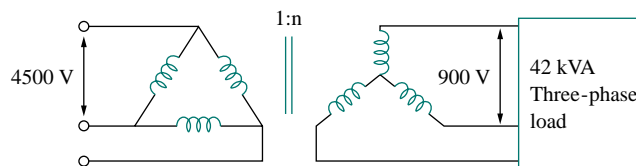


Figure 13.121 For Prob. 13.56.

**13.57** A Y- $\Delta$  three-phase transformer is connected to a 60-kVA load with 0.85 power factor (leading) through a feeder whose impedance is  $0.05 + j0.1 \Omega$  per phase, as shown in Fig. 13.122 below. Find the magnitude of:

- the line current at the load,
- the line voltage at the secondary side of the transformer,
- the line current at the primary side of the transformer.

**13.58** The three-phase system of a town distributes power with a line voltage of 13.2 kV. A pole transformer connected to single wire and ground steps down the high-voltage wire to 120 V rms and serves a house as shown in Fig. 13.123.

- Calculate the turns ratio of the pole transformer to get 120 V.
- Determine how much current a 100-W lamp connected to the 120-V hot line draws from the high-voltage line.

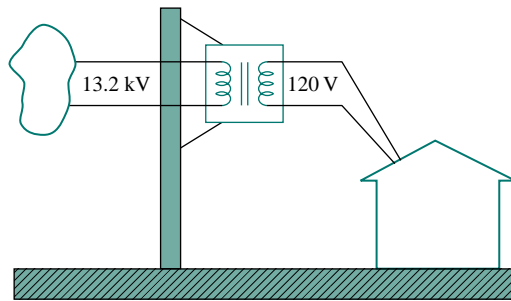


Figure 13.123 For Prob. 13.58.

### Section 13.8 PSpice Analysis of Magnetically Coupled Circuits

**13.59** Rework Prob. 13.14 using PSpice.

**13.60** Use PSpice to find  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit of Fig. 13.124.

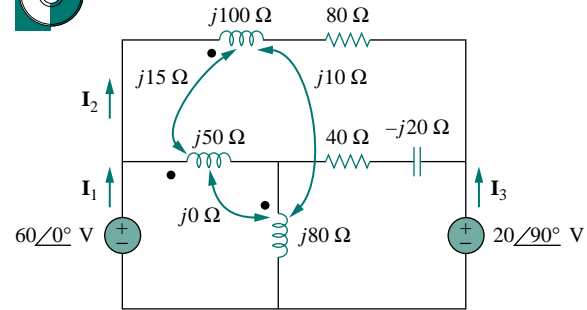


Figure 13.124 For Prob. 13.60.

**13.61** Rework Prob. 13.15 using PSpice.

**13.62** Use PSpice to find  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit of Fig. 13.125.

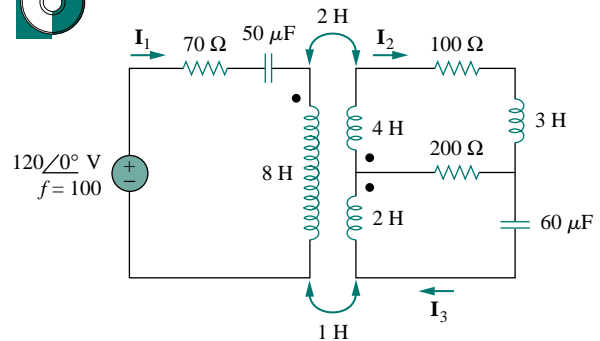


Figure 13.125 For Prob. 13.62.

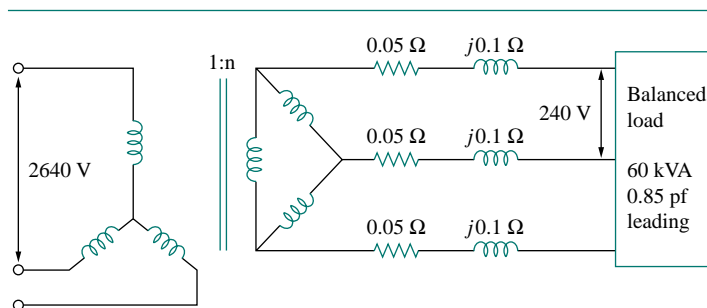


Figure 13.122 For Prob. 13.57.

- 13.63** Use *PSpice* to find  $V_1$ ,  $V_2$ , and  $I_o$  in the circuit of Fig. 13.126.

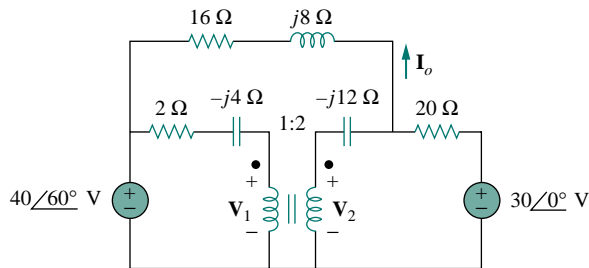


Figure 13.126 For Prob. 13.63.

- 13.64** Find  $I_x$  and  $V_x$  in the circuit of Fig. 13.127 below using *PSpice*.
- 13.65** Determine  $I_1$ ,  $I_2$ , and  $I_3$  in the ideal transformer circuit of Fig. 13.128 using *PSpice*.

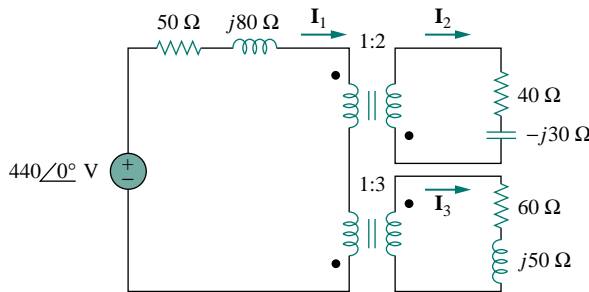


Figure 13.128 For Prob. 13.65.

**Section 13.9 Applications**

- 13.66** A stereo amplifier circuit with an output impedance of  $7.2 \text{ k}\Omega$  is to be matched to a speaker with an input impedance of  $8 \Omega$  by a transformer whose primary

side has 3000 turns. Calculate the number of turns required on the secondary side.

- 13.67** A transformer having 2400 turns on the primary and 48 turns on the secondary is used as an impedance-matching device. What is the reflected value of a  $3\text{-}\Omega$  load connected to the secondary?
- 13.68** A radio receiver has an input resistance of  $300 \Omega$ . When it is connected directly to an antenna system with a characteristic impedance of  $75 \Omega$ , an impedance mismatch occurs. By inserting an impedance-matching transformer ahead of the receiver, maximum power can be realized. Calculate the required turns ratio.
- 13.69** A step-down power transformer with a turns ratio of  $n = 0.1$  supplies  $12.6 \text{ V rms}$  to a resistive load. If the primary current is  $2.5 \text{ A rms}$ , how much power is delivered to the load?
- 13.70** A  $240/120\text{-V rms}$  power transformer is rated at  $10 \text{ kVA}$ . Determine the turns ratio, the primary current, and the secondary current.
- 13.71** A  $4\text{-kVA}$ ,  $2400/240\text{-V rms}$  transformer has 250 turns on the primary side. Calculate:  
 (a) the turns ratio,  
 (b) the number of turns on the secondary side,  
 (c) the primary and secondary currents.
- 13.72** A  $25,000/240\text{-V rms}$  distribution transformer has a primary current rating of  $75 \text{ A}$ .  
 (a) Find the transformer kVA rating.  
 (b) Calculate the secondary current.
- 13.73** A  $4800\text{-V rms}$  transmission line feeds a distribution transformer with 1200 turns on the primary and 28 turns on the secondary. When a  $10\text{-}\Omega$  load is connected across the secondary, find:  
 (a) the secondary voltage,  
 (b) the primary and secondary currents,  
 (c) the power supplied to the load.

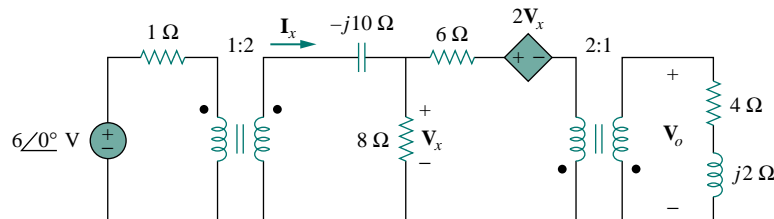


Figure 13.127 For Prob. 13.64.

## COMPREHENSIVE PROBLEMS

**13.74** A four-winding transformer (Fig. 13.129) is often used in equipment (e.g., PCs, VCRs) that may be operated from either 110 V or 220 V. This makes the equipment suitable for both domestic and foreign use. Show which connections are necessary to provide:

- an output of 12 V with an input of 110 V,
- an output of 50 V with an input of 220 V.

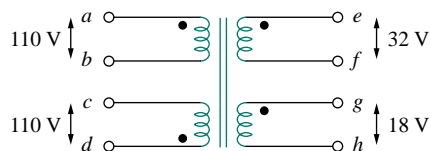


Figure 13.129 For Prob. 13.74.

**\*13.75** A 440/110-V ideal transformer can be connected to become a 550/440-V ideal autotransformer. There

are four possible connections, two of which are wrong. Find the output voltage of:

- a wrong connection,
- the right connection.

**13.76** Ten bulbs in parallel are supplied by a 7200/120-V transformer as shown in Fig. 13.130, where the bulbs are modeled by the  $144\text{-}\Omega$  resistors. Find:



- the turns ratio  $n$ ,
- the current through the primary winding.

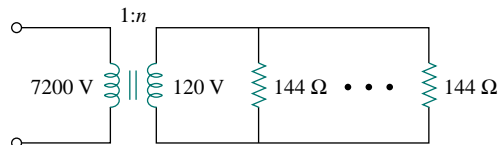


Figure 13.130 For Prob. 13.76.